

# **GENERAL ELECTRICAL ENGINEERING LAB**

## **TRANSISTOR CHARACTERISTICS**

**Experiment 5**

**CH-120-B**

**Location: Jacobs University Bremen, Research 1**

**Date: December 4<sup>th</sup>, 2020**

**Semester: 1**

**Group: Kuranage R R Ranasinghe, Abigail Christie**

**Kuranage R R Ranasinghe**

# Introduction

Explained in the simplest terms, a transistor is a device which controls the flow of electrons and hence, the electric current. When implemented in a circuit, these devices have two functions, i.e., they can either switch the direction of an electric current or amplify a current. This allows for more precise control of the electric current flowing through that circuit. Considering the structure of a transistor, it is made by placing two semi-conducting diodes 'back-to-back'. There are two types of transistors depending on the placement of the diodes (or P-N junctions) forming NPN or PNP type transistors. In a typical (bipolar) transistor, there are three terminals: the **emitter**, **base** and **collector**. When an electric current is applied at the central layer (**base**), electrons flow from the N-type side to the P-type side of the transistor. This small current applied acts as a switch which consequently allows a larger current to pass through, i.e., the transistor is acting as a switch and an amplifier at the same time in the circuit. A detailed drawing is given below.

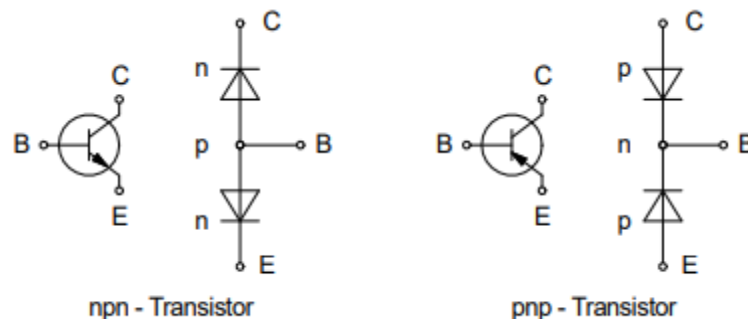


Fig. 1: A labelled Transistor (taken from lab manual)

A transistor can have different characteristics depending on its placement in the circuit. It can be forward bias, reverse bias or a current amplifier. During the experiment conducted, our focus is the **current amplification** characteristic.

# Experimental Set-up and Results

## Part 1: Input Characteristic

The following circuit was set up on the breadboard:

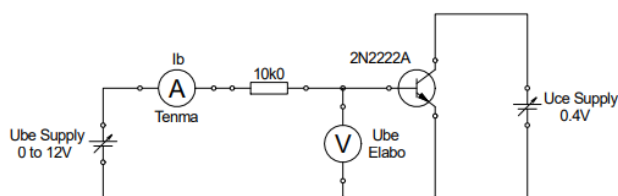


Fig. 2: Circuit to measure  $U_{BE}$  /  $I_{BE}$

The  $U_{ce}$  supply was set to 0.4V and the current was set using the Tenma ammeter to the following values consecutively: 0  $\mu A$ , 5  $\mu A$ , 10  $\mu A$ , 20  $\mu A$ , 40  $\mu A$ , 60  $\mu A$ , 80  $\mu A$ , 100  $\mu A$ , 200  $\mu A$ , 400  $\mu A$ , 600  $\mu A$ , 800  $\mu A$ , 1000  $\mu A$ .

Using the smallest possible range ( $\mu A$  in this case) on the Tenma multimeter, the set of  $I_{BE}$  from the ammeter and resulting  $U_{BE}$  from the voltmeter were recorded.

| Current ( $\mu A$ ) | $U_{BE}$ (V) | Current $I_{BE}$ (A) |
|---------------------|--------------|----------------------|
| 0                   | 0.0054       | 0                    |
| 4.87                | 0.6298       | 0.00000487           |
| 9.53                | 0.6485       | 0.00000953           |
| 19.93               | 0.6693       | 0.00001993           |
| 40.41               | 0.6895       | 0.00004041           |
| 59.55               | 0.7011       | 0.00005955           |
| 81.07               | 0.7105       | 0.00008107           |
| 99.84               | 0.7169       | 0.00009984           |
| 200.49              | 0.7417       | 0.00020049           |
| 399.95              | 0.77         | 0.00039995           |
| 597.5               | 0.7856       | 0.0005975            |
| 798.5               | 0.7964       | 0.0007985            |
| 1003.9              | 0.8077       | 0.0010039            |

Table 1: Results for forward bias


Next,  $U_{CE}$  was disconnected and the  $U_{BE}$  supply was reversed. The reverse current  $I_{BR}$  was then recorded as a function of  $U_{BE}$ .

| Current ( $\mu A$ ) | $U_{BE}$ (V) | Current $I_{BR}$ (A) |
|---------------------|--------------|----------------------|
| 0                   | -0.009       | 0.00000000           |
| -4.93               | -8.126       | -0.00000493          |
| -9.72               | -8.127       | -0.00000972          |
| -20.39              | -8.129       | -0.00002039          |
| -41.18              | -8.13        | -0.00004118          |
| -60.44              | -8.131       | -0.00006044          |
| -79.07              | -8.132       | -0.00007907          |
| -100.43             | -8.133       | -0.00010043          |
| -199.52             | -8.135       | -0.00019952          |
| -400.8              | -8.141       | -0.00040080          |
| -602.6              | -8.149       | -0.00060260          |
| -805.8              | -8.157       | -0.00080580          |
| -1001.5             | -8.166       | -0.00100150          |

Table 2: Results for reverse bias
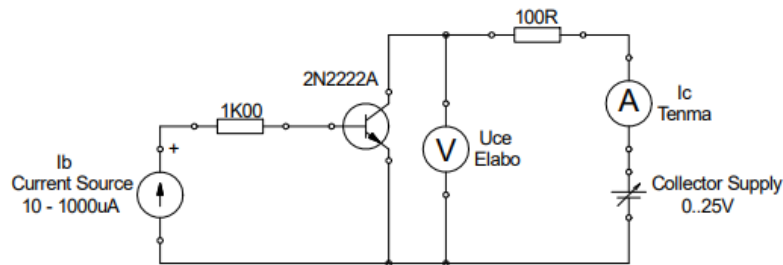
## Part 2: Output Characteristic

The next circuit was set up as shown in Fig. 3.



The constant current source is the small black box in the shelf of the workbench labeled "Current  $\mu A$ ". Plug it into one of the outputs of the DC-supply. Set the voltage to 20V. The output of the source is the BNC-plug at the bottom. Use the BNC to Cleps cable to connect it to the circuit. The red wire of the BNC-cable is the positive terminal and the black wire is the ground.

Fig. 3: Set-up for Part 2 of experiment (taken from Lab Manual)

For this part,  $I_B$  was set to  $20\mu\text{A}$  and the collector supply was varied in a way that  $U_{CE}$  (read from Elabo) was changed from 0 V to 20 V in consecutive steps:

- from 0 V to 1 V every 0.2 V
- then 2.5 V, 5 V, 10 V, 15 V, and 20 V

The values of  $U_{CE}$  and  $I_{CE}$  had to be recorded quickly since the transistor heats up and will change its characteristics. (a smartphone camera was used to take a snapshot of the readings of the circuit at all the steps to get more accurate results and allow for faster data collection.) The whole experiment was done in such a way that  $P_{CE} = U_{CE} * I_{CE} = 700 \text{ mW}$  was never exceeded.

- the first step was repeated for  $I_B = 40 \mu\text{A}$ ,  $60 \mu\text{A}$ ,  $80 \mu\text{A}$ , and  $100 \mu\text{A}$ .
- $I_{CE}$  was recorded for  $I_B = 100 \mu\text{A}$ ,  $200 \mu\text{A}$ ,  $300 \mu\text{A}$ ,  $400 \mu\text{A}$  and  $500 \mu\text{A}$  with  $U_{CE}$  set to 1 V.

All results are recorded below in tables.

| Steps | $U_{CE}$ (V) | $I_{CE}$ (A) | Power(W) |
|-------|--------------|--------------|----------|
| 0     | 0.01         | 1.64E-04     | 1.64E-06 |
| 0.2   | 0.206        | 4.23E-03     | 8.72E-04 |
| 0.4   | 0.403        | 4.28E-03     | 1.72E-03 |
| 0.6   | 0.602        | 4.30E-03     | 2.59E-03 |
| 0.8   | 0.817        | 4.32E-03     | 3.53E-03 |
| 1     | 1.06         | 4.38E-03     | 4.64E-03 |
| 2.5   | 2.514        | 4.43E-03     | 1.11E-02 |
| 5     | 5.01         | 4.57E-03     | 2.29E-02 |
| 10    | 10.12        | 4.87E-03     | 4.93E-02 |
| 15    | 15.046       | 5.20E-03     | 7.83E-02 |
| 20    | 20.03        | 5.69E-03     | 1.14E-01 |

Table 3: Results for  $I_B = 20 \mu\text{A}$

| Step | $U_{ce}$ (V) | $I_{ce}$ (A) | Power(W) |
|------|--------------|--------------|----------|
| 0    | 0            | 9.70E-05     | 0.00E+00 |
| 0.2  | 0.19         | 9.30E-03     | 1.77E-03 |
| 0.4  | 0.38         | 9.43E-03     | 3.58E-03 |
| 0.6  | 0.61         | 9.35E-03     | 5.70E-03 |
| 0.8  | 0.8          | 9.33E-03     | 7.46E-03 |
| 1    | 1.02         | 9.33E-03     | 9.52E-03 |
| 2.5  | 2.51         | 9.49E-03     | 2.38E-02 |
| 5    | 5.01         | 9.85E-03     | 4.94E-02 |
| 10   | 10.01        | 1.08E-02     | 1.08E-01 |
| 15   | 15.08        | 1.21E-02     | 1.83E-01 |
| 20   | 20.1         | 1.37E-02     | 2.74E-01 |

Table 4: Results for  $I_B = 40 \mu A$

| STEP | $U_{ce}$ (V) | $I_{ce}$ (A) | Power(W) |
|------|--------------|--------------|----------|
| 0    | 0            | 2.20E-04     | 0.00E+00 |
| 0.2  | 0.21         | 1.29E-02     | 2.70E-03 |
| 0.4  | 0.4          | 1.31E-02     | 5.25E-03 |
| 0.6  | 0.62         | 1.32E-02     | 8.20E-03 |
| 0.8  | 0.79         | 1.33E-02     | 1.05E-02 |
| 1    | 1.05         | 1.35E-02     | 1.41E-02 |
| 2.5  | 2.49         | 1.39E-02     | 3.46E-02 |
| 5    | 5.12         | 1.49E-02     | 7.61E-02 |
| 10   | 10.05        | 1.70E-02     | 1.71E-01 |
| 15   | 15.08        | 1.98E-02     | 2.98E-01 |
| 20   | 20.02        | 2.29E-02     | 4.59E-01 |

Table 5: Results for  $I_B = 60 \mu A$

| STEP | $U_{ce}$ (V) | $I_{ce}$ (A) | Power(W) |
|------|--------------|--------------|----------|
| 0    | 0.161        | 0.00E+00     | 0.00E+00 |
| 0.2  | 0.19         | 1.69E-02     | 3.21E-03 |
| 0.4  | 0.4          | 1.75E-02     | 7.00E-03 |
| 0.6  | 0.59         | 1.76E-02     | 1.04E-02 |
| 0.8  | 0.78         | 1.78E-02     | 1.39E-02 |
| 1    | 1.01         | 1.80E-02     | 1.81E-02 |
| 2.5  | 2.55         | 1.88E-02     | 4.81E-02 |
| 5    | 5.21         | 2.03E-02     | 1.06E+02 |
| 10   | 10.02        | 2.38E-02     | 2.38E-01 |
| 15   | 14.99        | 2.80E-02     | 4.19E-01 |
| 20   | 20.28        | 3.24E-02     | 6.58E-01 |

Table 6: Results for  $I_B = 80 \mu A$

| STEP | $U_{ce}$ (V) | $I_{ce}$ (A) | Power(W) |
|------|--------------|--------------|----------|
| 0    | 0            | 2.33E-04     | 0.00E+00 |
| 0.2  | 0.2          | 2.10E-02     | 4.20E-03 |
| 0.4  | 0.42         | 2.19E-02     | 9.18E-03 |
| 0.6  | 0.61         | 2.21E-02     | 1.35E-02 |
| 0.8  | 0.79         | 2.23E-02     | 1.76E-02 |
| 1    | 1.02         | 2.25E-02     | 2.30E-02 |
| 2.5  | 2.52         | 2.39E-02     | 6.01E-02 |
| 5    | 5.03         | 2.66E-02     | 1.34E-01 |
| 10   | 10.03        | 3.30E-02     | 3.31E-01 |
| 15   | 15.05        | 3.98E-02     | 5.99E-01 |
| 20   |              |              |          |

Table 7: Results for  $I_B = 100 \mu A$

**Note:** No reading was taken for the 20V step when  $I_B$  was set to 100  $\mu\text{A}$  as the power exceeded the maximum value of 700mW

Finally,  $I_{CE}$  was recorded for  $I_B = 100 \mu\text{A}$ , 200  $\mu\text{A}$ , 300  $\mu\text{A}$ , 400  $\mu\text{A}$ , and 500  $\mu\text{A}$  with  $U_{CE}$  set to 1 V. It was ensured that  $U_{CE}$  was adjusted every time after changing  $I_B$ .

| $I_B$    | $I_{ce}$ |
|----------|----------|
| 1.00E-04 | 2.27E-02 |
| 2.00E-04 | 4.55E-02 |
| 3.00E-04 | 6.88E-02 |
| 4.00E-04 | 9.18E-02 |
| 5.00E-04 | 1.13E-01 |


Table 8: Results for different  $I_B$

## Evaluation

### PART 1: Input Characteristic

#### Forward Bias


| $U_{BE}$ (V) | Current $I_{BE}$ (A) |
|--------------|----------------------|
| 0.0054       | 0                    |
| 0.6298       | 0.00000487           |
| 0.6485       | 0.00000953           |
| 0.6693       | 0.00001993           |
| 0.6895       | 0.00004041           |
| 0.7011       | 0.00005955           |
| 0.7105       | 0.00008107           |
| 0.7169       | 0.00009984           |
| 0.7417       | 0.00020049           |
| 0.77         | 0.00039995           |
| 0.7856       | 0.0005975            |
| 0.7964       | 0.0007985            |
| 0.8077       | 0.0010039            |

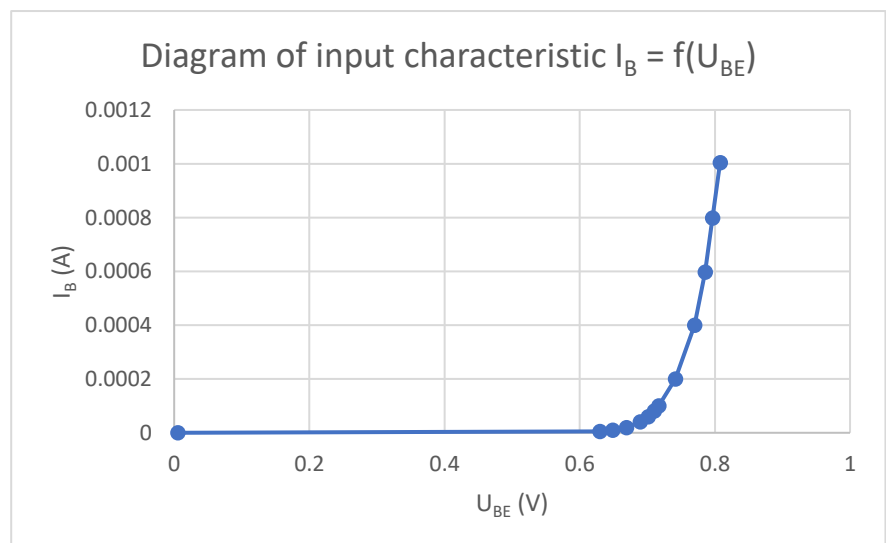




## Reverse Bias

| $U_{BE}$ (V) | Current $I_{BR}$ (A) |
|--------------|----------------------|
| -0.009       | 0.00000000           |
| -8.126       | -0.00000493          |
| -8.127       | -0.00000972          |
| -8.129       | -0.00002039          |
| -8.13        | -0.00004118          |
| -8.131       | -0.00006044          |
| -8.132       | -0.00007907          |
| -8.133       | -0.00010043          |
| -8.135       | -0.00019952          |
| -8.141       | -0.00040080          |
| -8.149       | -0.00060260          |
| -8.157       | -0.00080580          |
| -8.166       | -0.00100150          |

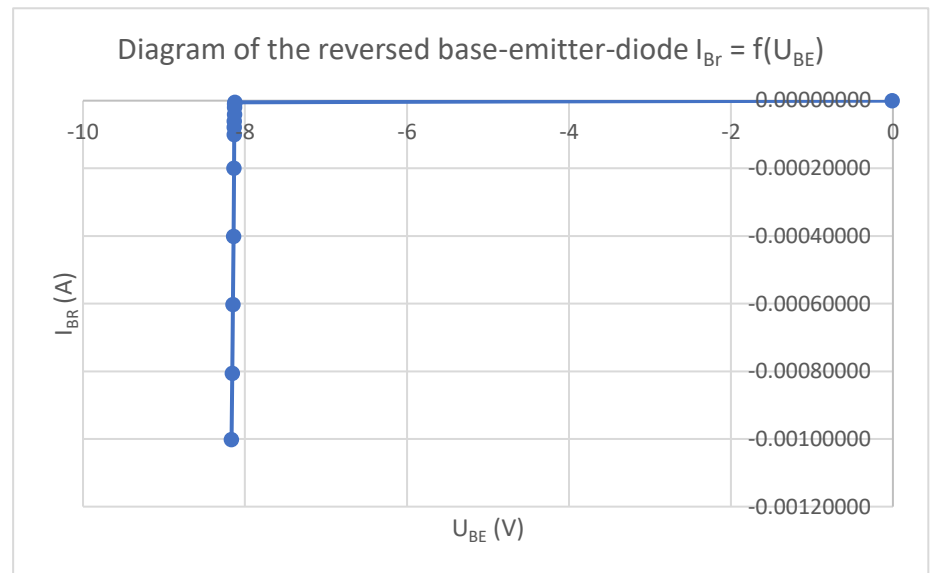

## Comparison to the diode curves from the diode experiment


### Forward Bias Comparison:

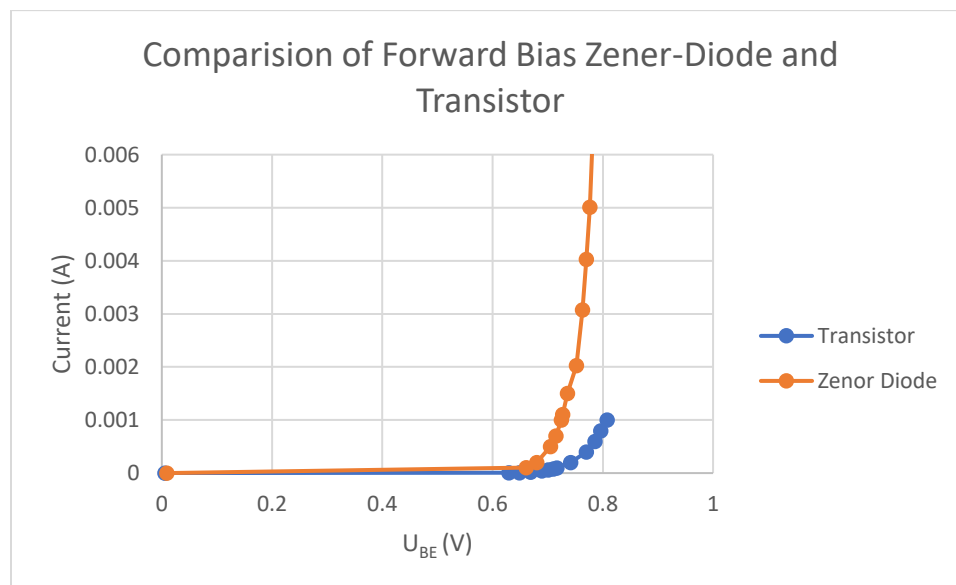

According to the chart, both the Zener-Diode and the transistor have similar forward bias characteristics. However, the transistor goes through forward bias at a higher voltage than the Zener-Diode. During forward bias, the Zener-Diode lets through a larger current over a small voltage variation when compared to the

transistor. This conclusion can be reached by observing the much steeper gradient of the Zener-Diode. (some data collected for the Zener-diode has been ignored since it exceeds the y-axis scale here)


### Reverse Bias Comparison:

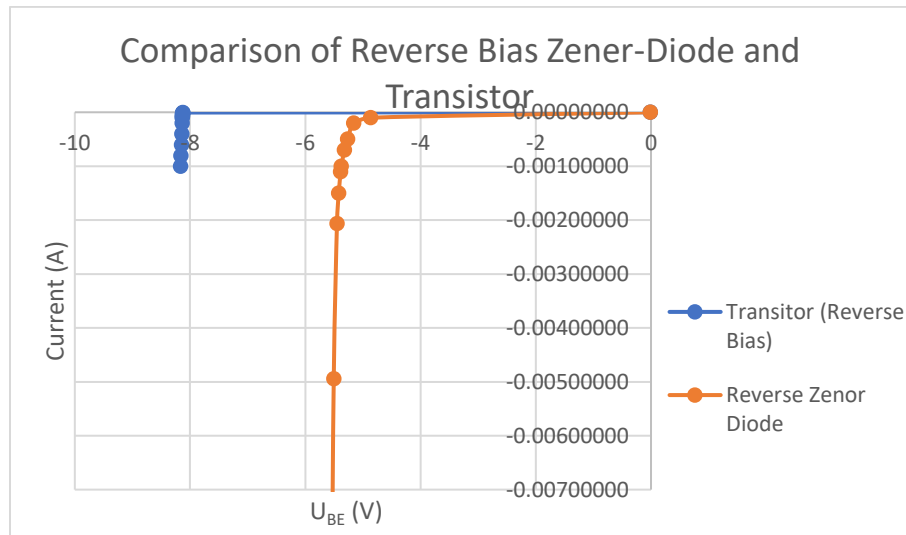


According to this graph, the transistor in reverse bias has a greater negative breakdown voltage than the Zener-Diode in reverse bias. Once again, by analyzing the steepness of the graphs, it is obvious that the transistor in reverse bias (which has the steeper gradient) conducts a larger current over a small voltage variation. (some data collected for the Zener-diode in reverse bias has been ignored since it exceeds the y-axis scale here)

The differences observed in the characteristics of these two devices is very likely due to the structural difference between them (diodes have a single P-N junction while transistors have two), although the difference in circuit set up could also be a factor.

## Part 2: Output Characteristic

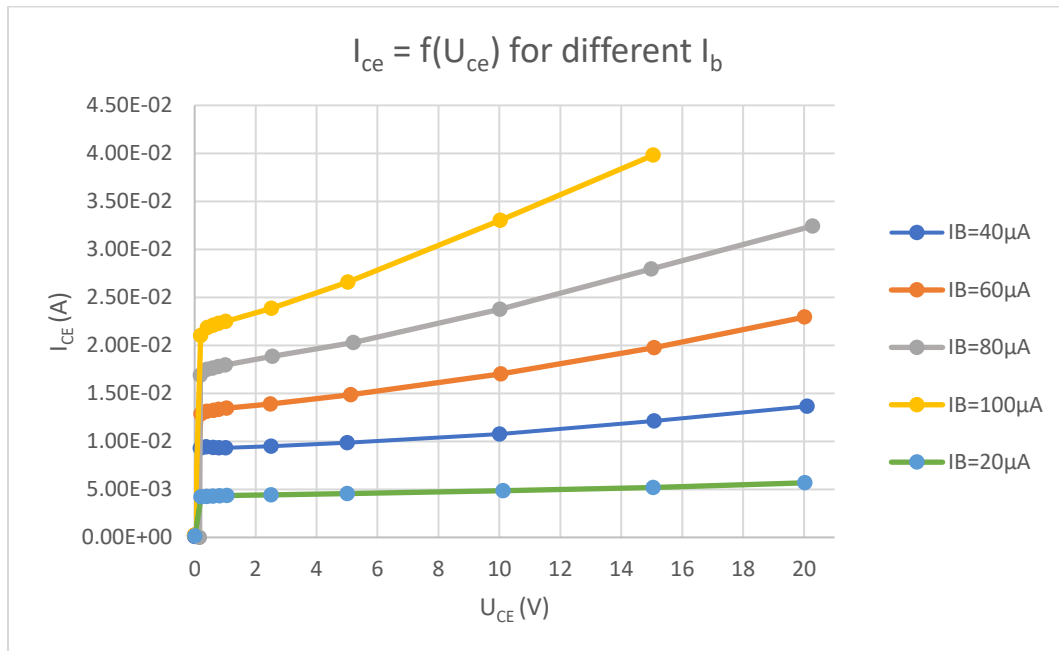


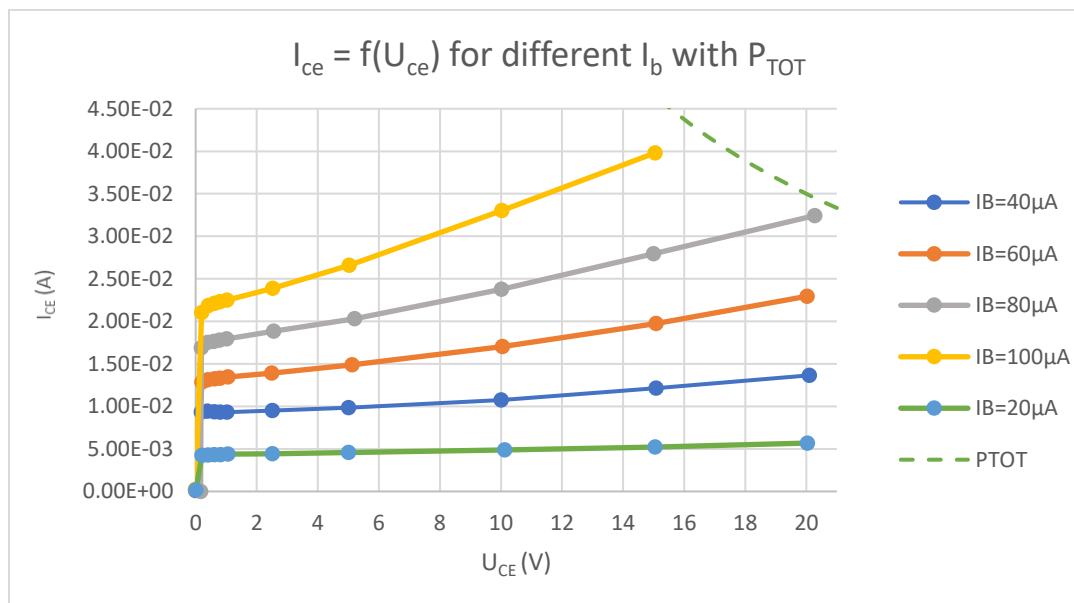Since the maximum power dissipation for the **2N2222** is  $P_{TOT} = 700$  mW, the line for  $P_{TOT}$  is included in the graph as shown below.



According to the graph, it is clear that the limit was NOT exceeded at any point during the experiment. However, if the value at 20V  $U_{CE}$  was taken into account for when  $I_B = 100 \mu A$ , it would have clearly exceeded the maximum power dissipation of the particular diode.

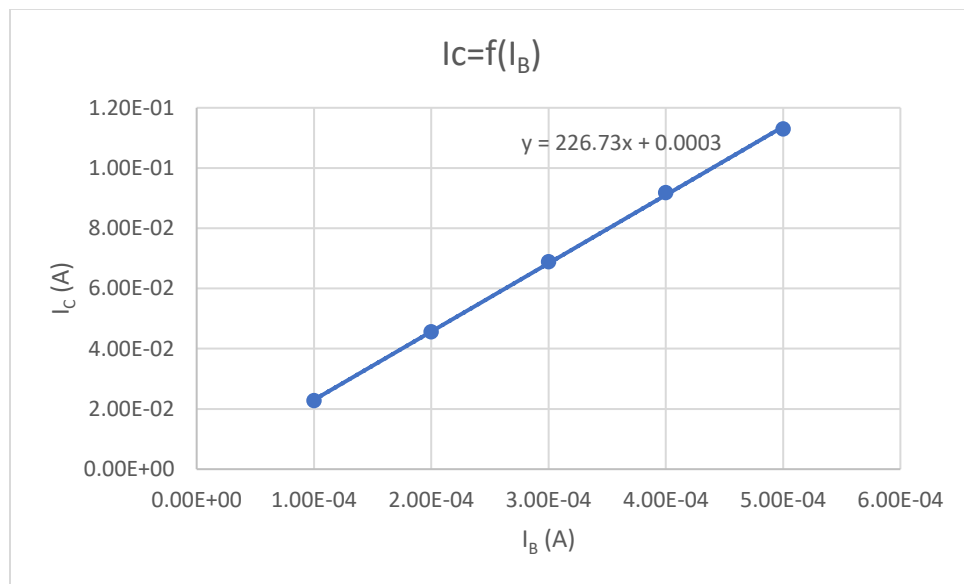When  $U_{CE} = 1V$  (constant), the following graph could be plotted on excel for  $I_C = f(I_B)$ . Analyzing the straight trendline plotted, it was found that the equation of the graph is  $y = 226.73x + 0.0003$ .



Current Amplification for this experiment can be found using the following formula:

$$\text{Current Amplification} = \frac{I_C}{I_B}$$


An example calculation when  $I_C = 22.693 \text{ mA}$  and  $I_B = 0.100 \text{ mA}$ :

$$\text{Current Amplification} = \frac{22.693}{0.100} = 226.93$$

Other values obtained are given below:

| $I_B$    | $I_C$    | Current Amplification |
|----------|----------|-----------------------|
| 1.00E-04 | 2.27E-02 | 226.93                |
| 2.00E-04 | 4.55E-02 | 227.7                 |
| 3.00E-04 | 6.88E-02 | 229.367               |
| 4.00E-04 | 9.18E-02 | 229.45                |
| 5.00E-04 | 1.13E-01 | 225.88                |

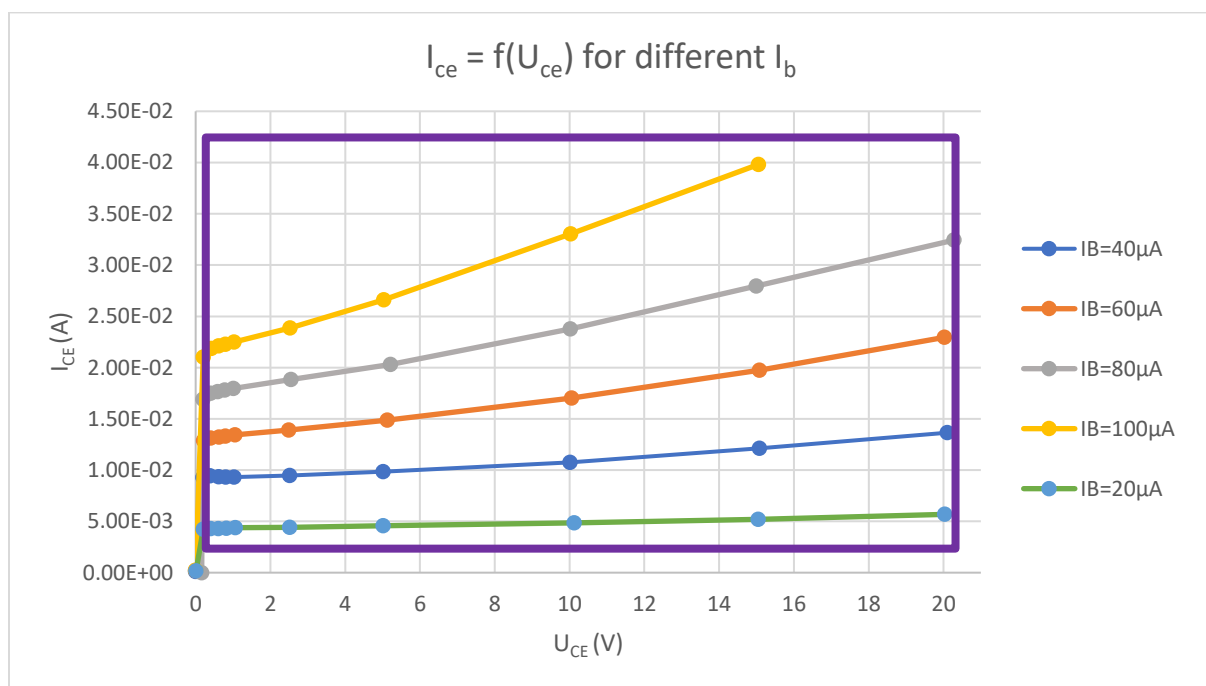The Area for which linear operation is possible is indicated by the purple box in the diagram below:



# Conclusion

Throughout this experiment, the characteristics of a transistor were our main points of focus. This involved exploring the forward and reverse bias characteristics. These characteristics were then compared to those of a Zener-Diode used in the previous experiment. From the analysis of both sets of results, the conclusion drawn was that while both showed similar characteristics, there were some differences which were observed through the gradient of the graphs. The transistor conducted a large amount of current within a small voltage variation than a diode.

For the next part where the use of a transistor as an amplifier were shown:

- For an NPN transistor, the emitter current was the sum of the collector current and the base current ( $I_E = I_C + I_B$ ). The amplification of the current is  $I_C/I_B$ .

During this evaluation, the area in which a transistor could perform linear operations was also covered. This is an important property of transistor amplification since nonlinear amplification causes distortion. Hence, linear amplification is preferred.

The threshold power of transistors was also explored since the transistor we used (2N2222) could not go beyond 700 mW. However, since the power was always kept below this limit and since all high-power measurements were done quickly and recorded, there was no damage to the transistor used.

The only major error source was that if the measurements were not taken fast enough, the values would be erroneous due to heating of the transistor, but this was also avoided by taking pictures of the results instead of reading them off the instruments.

# References

[Lab Manual \(jacobs-university.de\)](http://jacobs-university.de)

<https://www.build-electronic-circuits.com/how-transistors-work/>

## Appendix


### Data collected from Ohm's Law Lab, done on: Dec 3, 2020

#### PART 1: Determine Anode and Cathode

- Ring points to positive (Reverse Bias)  
V=12.067V  
A=1.11 $\mu$ A
- Ring points to negative (Forward Bias)  
V=0.7268V  
A= 20.079mA

#### Part 2: Forward V-I-Curve of a general purpose diode


| V      | A        |
|--------|----------|
| 0.0087 | 0.00E+00 |
| 0.4536 | 5.06E-05 |
| 0.4811 | 1.01E-04 |
| 0.5111 | 2.01E-04 |
| 0.5537 | 5.05E-04 |
| 0.5866 | 1.00E-03 |
| 0.6212 | 2.01E-03 |
| 0.6415 | 3.00E-03 |
| 0.6553 | 4.00E-03 |
| 0.6657 | 5.02E-03 |
| 0.6975 | 1.00E-02 |
| 0.7272 | 2.00E-02 |
| 0.7557 | 4.00E-02 |

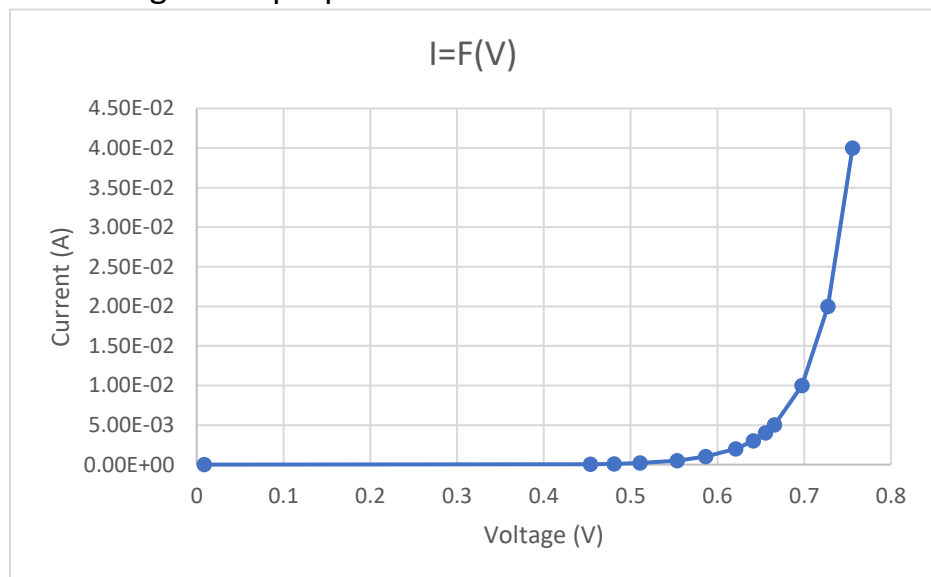

### Part 3: Reverse and Forward Characteristic of a Z-Diode


#### Reverse Zener Diode

| v       | A        |
|---------|----------|
| VOLTAGE | CURRENT  |
| 0.0088  | 0        |
| 4.865   | 1.01E-04 |
| 5.16    | 2.02E-04 |
| 5.263   | 5.00E-04 |
| 5.321   | 6.99E-04 |
| 5.373   | 1.00E-03 |
| 5.385   | 1.10E-03 |
| 5.42    | 1.50E-03 |
| 5.45    | 2.07E-03 |
| 5.506   | 4.94E-03 |
| 5.544   | 1.01E-02 |
| 5.588   | 2.01E-02 |
| 5.663   | 4.00E-02 |
| 5.679   | 4.50E-02 |

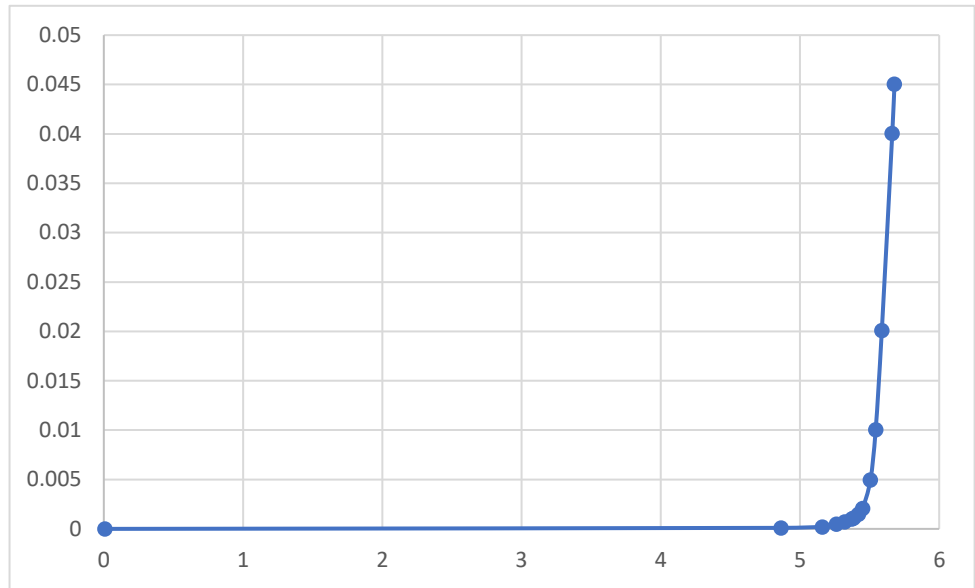

#### Forward Bias Zener Diode

| V      | A        |
|--------|----------|
| 0.0088 | 0        |
| 0.661  | 0.000102 |
| 0.68   | 0.000201 |
| 0.705  | 0.000499 |
| 0.715  | 0.000699 |
| 0.725  | 0.001002 |
| 0.727  | 0.001101 |
| 0.736  | 0.0015   |
| 0.752  | 2.03E-03 |
| 0.763  | 3.08E-03 |
| 0.7699 | 4.03E-03 |
| 0.7762 | 5.01E-03 |
| 0.7955 | 1.00E-02 |
| 0.8073 | 1.51E-02 |

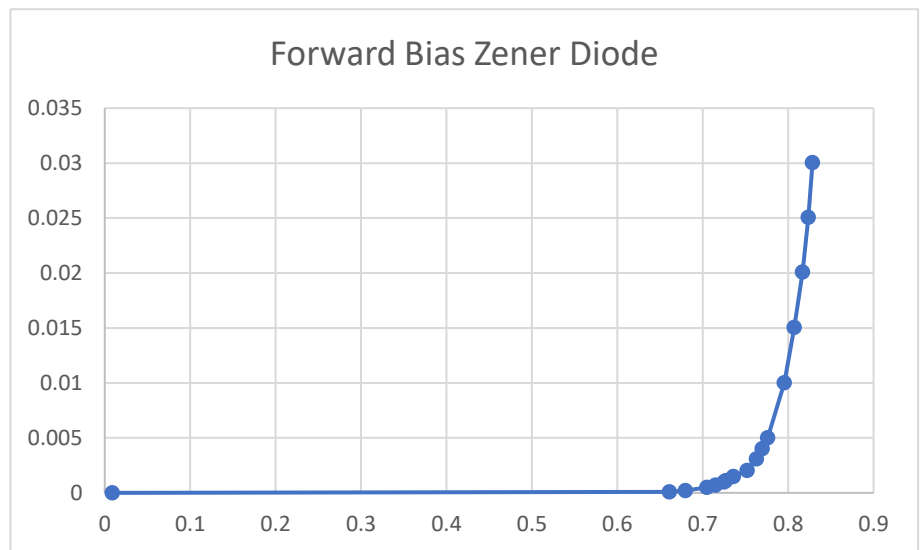



|        |          |
|--------|----------|
| 0.8168 | 2.01E-02 |
| 0.8236 | 2.51E-02 |
| 0.8286 | 3.01E-02 |

#### Part 4: A Zener Shunt Regulator

| I <sub>z</sub> =1mA, R= 855 Ω |          |         |
|-------------------------------|----------|---------|
| Load (Ohms)                   | I (Amps) | V(Volt) |
| 56                            | 1.63E-02 | 0.917   |
| 560                           | 1.11E-02 | 5.414   |
| 5600                          | 1.10E-02 | 5.54    |
| No RL                         | 1.10E-02 | 5.546   |

| I <sub>z</sub> =10mA, R= 470Ω |          |       |
|-------------------------------|----------|-------|
| 56                            | 2.81E-02 | 1.58  |
| 560                           | 1.99E-02 | 5.54  |
| 5600                          | 1.98E-02 | 5.58  |
| No RL                         | 1.98E-02 | 5.583 |